

Electric current: experimenting with circuits

Name: _____

Electric circuit symbols




Wire



Bulb



Battery

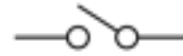

Switch

Draw your circuits, using the symbols. **Write** what happens in each case.